

## Lab 3 Manual

### 1 Objectives

Understand feedback control.

### 2 What to Bring

Each group should bring a USB storage device to store the screen image.

### 3 Open Loop Control—Plant

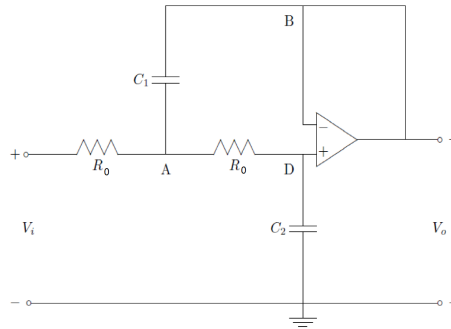


Figure 1: Plant Circuit

Steps:

1. Construct the plant circuit according to Figure 1. Where  $R_0 = 10k\Omega$ ,  $C_1 = 100\mu F$ ,  $C_2 = 0.22\mu F$ .
2. Impulse response:  $A=1V$ , width=0.1s,  $f=1Hz$ . (1 Picture)
3. Step Response:  $A=1V$ ,  $f=1Hz$ . (1 Picture)

For example, for the step response, you should try to get something like the waveform shown in following figure.

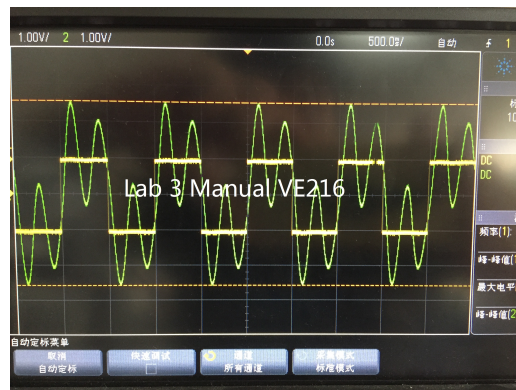


Figure 2: Plant Result

**Note 1:** Do not destroy your plant circuit after you get the image, you are going to use it in the next part.

Note 2: Do not forget to supply all the op-amps with DC voltage(Pin 4(-12V) and 7(12V))

Note 3: If a capacitor is labeled “474”, its capacitance is  $47 \times 10^4 \text{ pF}$ ; “224” is  $22 \times 10^4 \text{ pF}$

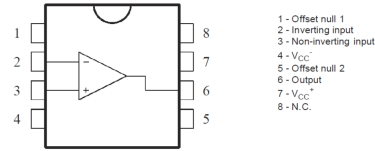


Figure 3: Op-amp

## 4 Feedback Control

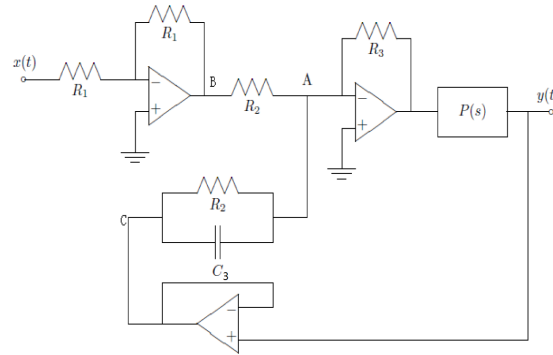


Figure 4: Feedback Control Circuit

Steps:

1. Add the feedback control circuit to the plant according to Figure 3. Where  $R_1 = R_3 = 150k\Omega$ ,  $R_2 = 3k\Omega$ ,  $C_3 = 0.47\mu F$ .
2. Impulse response:  $A=1V$ , width=0.1s,  $f=1Hz$ . (1 Picture)
3. Step Response:  $A=1V$ ,  $f=1Hz$ . (1 Picture)

For example, for step response, you should try to get something like the waveform shown in the following figure.

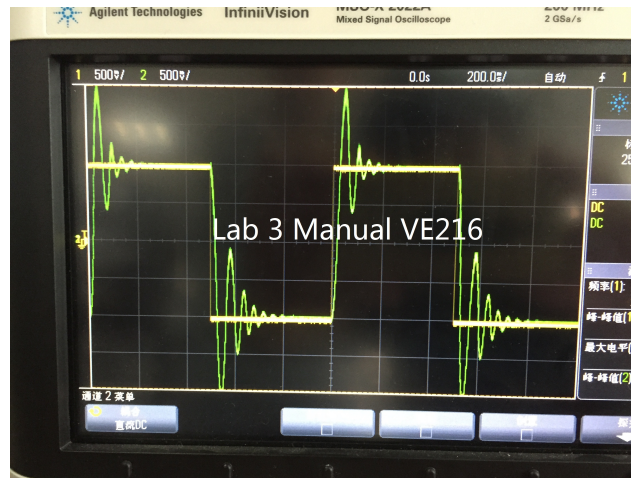


Figure 5: Feedback Control Result